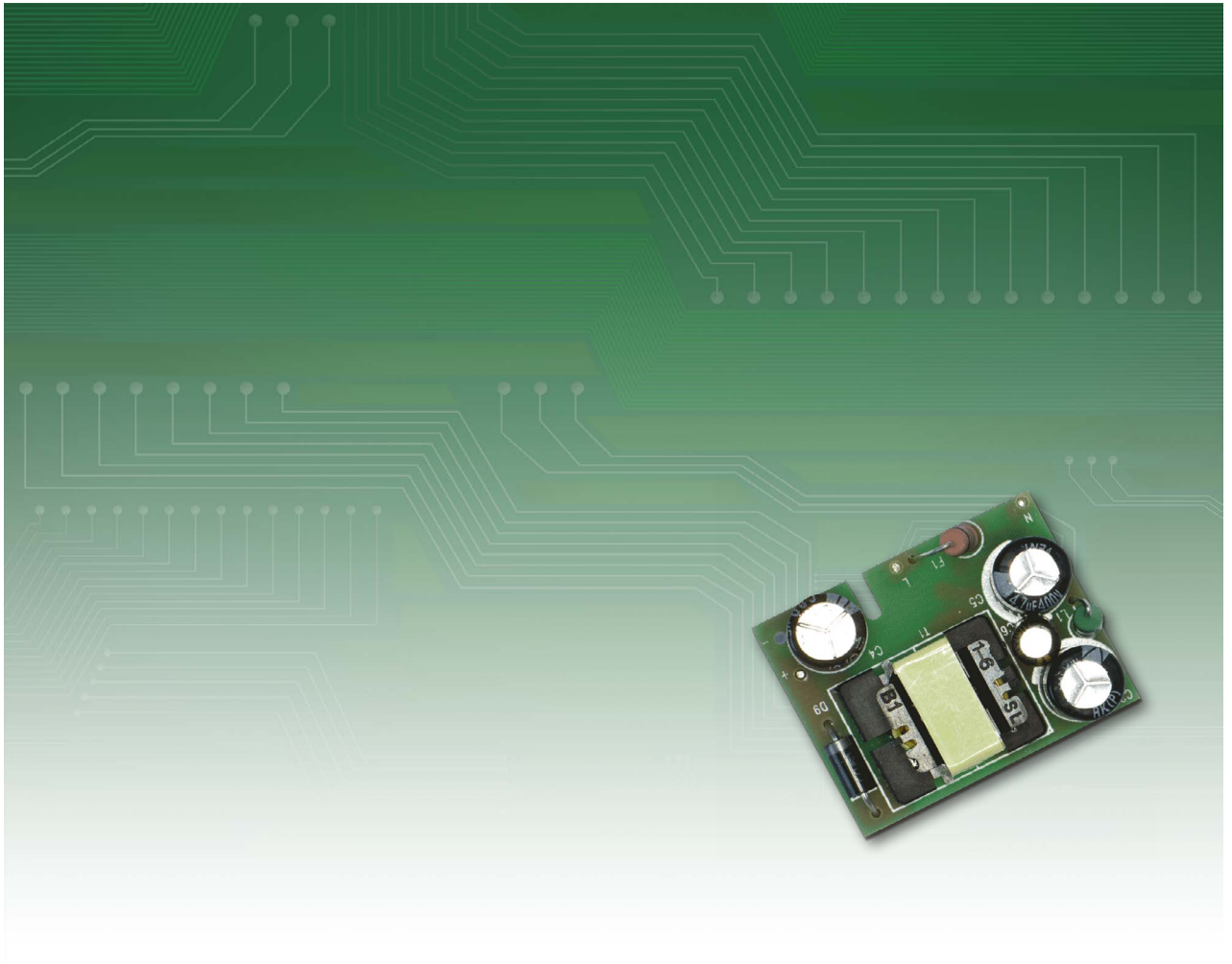


Reference Design

**EBC10013**

**iWatt**<sup>®</sup>  
Power Management Simplified Digitally™



**iW1810-00 For 5V 600mA  
AC-DC SMPS Design**

# iW1810-00 For AC-DC SMPS Design (AC Input 90–264V<sub>AC</sub>, Output 5V 600mA) EBC10013

1.0. Introduction .....	3
2.0. Design Features .....	3
3.0. Power Supply Design Specification .....	4
4.0. Schematic .....	5
5.0. PCB Layout.....	5
6.0. Bill Of Materials.....	6
7.0. Transformer Drawing .....	7
8.0. Performance .....	8
8.1. Regulation, Ripple and Efficiency Measurement.....	8
8.2. CV and CC Regulation .....	8
8.3. Conducted EMI .....	8

## 1.0 Introduction

This document provides a reference design for a universal input, 5V 600mA isolated flyback switched-mode power supply. For this design the iW1810-00 is used. This document contains the complete specification of the power supply, a detailed circuit diagram, an entire bill of materials required to build the power supply, a drawing of the power transformer, and test data of the most important performance.




AC Input

Figure 1.1 PCB Top View



Figure 1.3 Side View

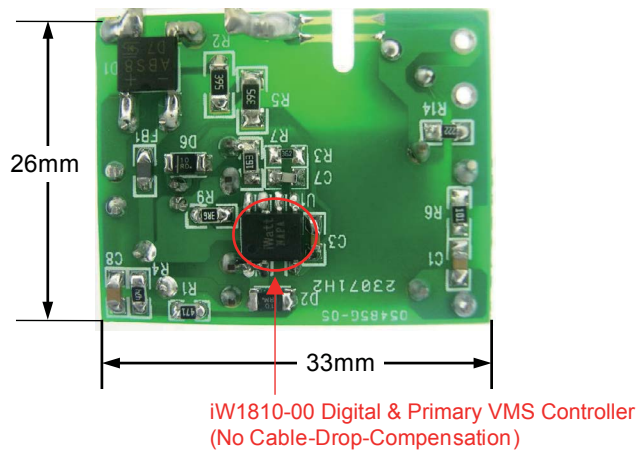

iW1810-00 Digital & Primary VMS Controller  
(No Cable-Drop-Compensation)

Figure 1.2 PCB Bottom View

## 2.0 Design Features

- AC input range 90-264V<sub>AC</sub>
- DC output 5V 600-800mA
- Meet “100mW” no-load standby power consumption requirement
- Meet “EPA 2.0” requirement
- Max ripple <150mV<sub>P-P</sub>

### 3.0 Power Supply Design Specification

The information in the table below represents the minimum acceptable performance of the design.

Description	Symbol	Min	Typ	Max	Units	Comment	
<b>Input</b>							
Voltage	$V_{IN}$	90		264	$V_{AC}$	2 wire	
Frequency	$f_{LINE}$	47	50/60	63	Hz		
No-load input power (230V <sub>AC</sub> )				100	mW		
<b>Output</b>							
Constant voltage	Output voltage	$V_{OUT_{CV}}$	4.75	5.00	5.25	V	Measured at end of PCB
	Output current	$I_{OUT_{CV}}$	0		0.60	A	
Constant current	Output voltage	$V_{OUT_{CC}}$	2.5	Depending on battery voltage		V	Min $V_{OUT}$ is dependent on $V_{CC}$ supply voltage
	Output current	$I_{OUT_{CC}}$	0.60		0.80	A	
Output ripple voltage	$V_{RIPPLE}$			150	mV <sub>P-P</sub>	Measured at end of PCB $I_{OUT}=0.6A @T_A=25^{\circ}C$ 20MHz bandwidth	
<b>Total Output Power</b>							
Continuous output power	$P_{OUT}$		3		W		
Over-current protection	$I_{OUT_{MAX}}$			0.80	A	Auto-restart	
Active mode efficiency (meet EPA2.0)	$\eta$	64.4			%	Measured at end of PCB, $V_{IN}=115V_{AC}$ and $230V_{AC}$ ( $T_{AMB}=25^{\circ}C$ )	
<b>Environmental</b>							
Conducted EMI		Meets CISPR22B/EN55022B					
Safety		Designed to meet IEC950, UL1950 Class II					
Ambient temperature	$T_{AMB}$	0		40	°C	Free convection, sea level	

4.0 Schematic

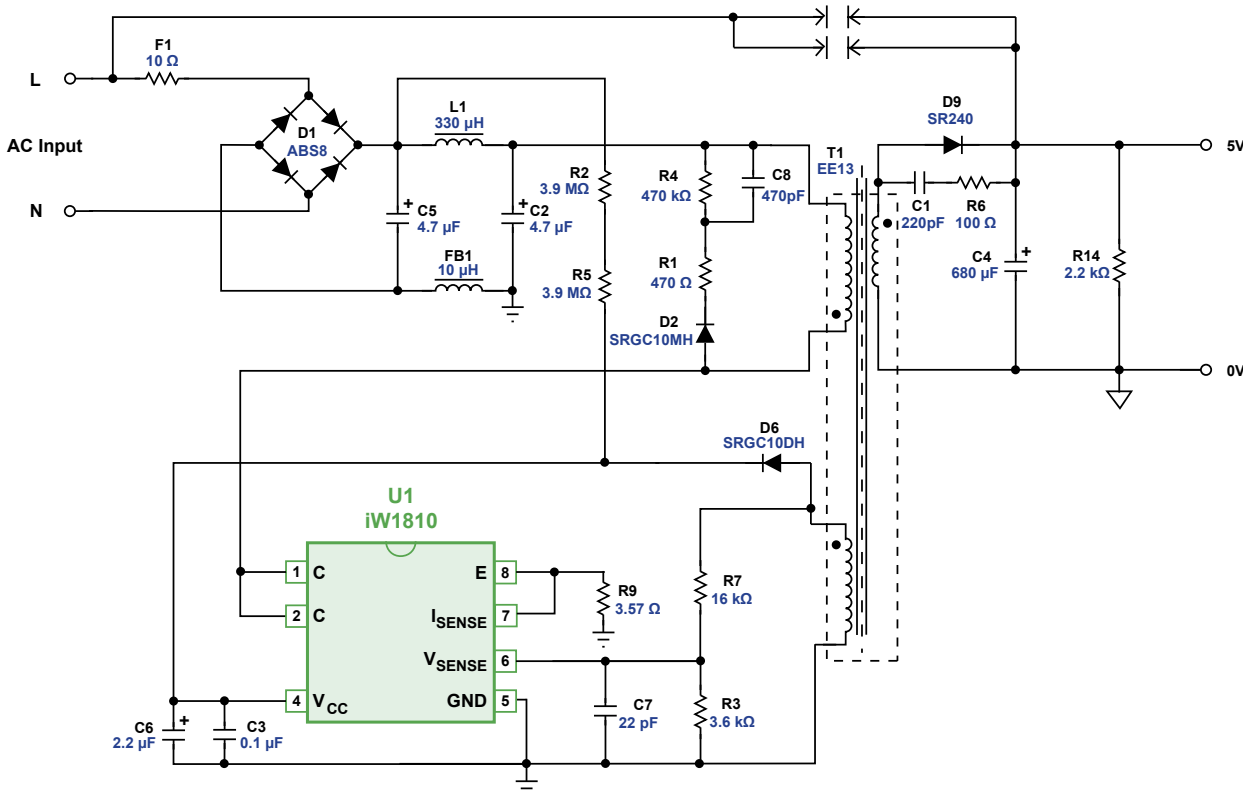


Figure 4.1 Design Schematic

5.0 PCB Layout

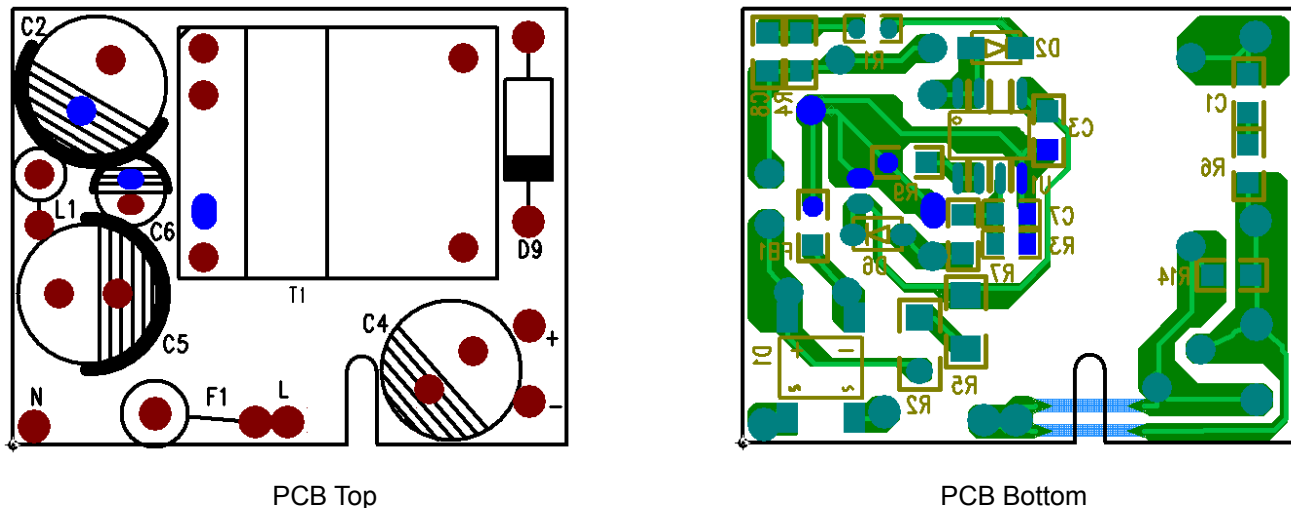


Figure 5.1 PCB Layout 33.0 mm x 26.0 mm


www.iwatt.com

## 6.0 Bill of Materials

Item	Qty.	Ref.	Description	Manufacturer P/N	Manufacturer
1	1	U1	iW1810-00, off-line digital&primary VMS controller, SOIC-7	iW1810-00	iWatt, Inc
2	1	C1	220pF, 100V, X7R, SMD-0805	08051C221KAT2A	AVX Corporation
3	2	C2,C5	4.7μF, 400V, E-CAP, (Φ8mm×12mm)	KLH-400V4R7MF120	KOSHIN
4	1	C3	100nF, 25V, X7R, SMD-0603	C1608X7R1E104K	TDK Corporation
5	1	C4	680μF, 10V, E-CAP, low ESR, (Φ8mm×12mm)	KLH-010V681MF120	KOSHIN
6	1	C6	2.2μF, 50V, E-CAP, low ESR, (Φ5mm×11mm)	KLH-050V2R2MF110	KOSHIN
7	1	C7	22pF, NPO, 25V, SMD-0603	06033A220JAT2A	AVX Corporation
8	1	C8	470pF, 250V, X7R, SMD-0805	0805VC471KAT2A	AVX Corporation
9	1	R1	470Ω ±5%, SMD-0805	ERJ-6GEYJ471V	Panasonic - ECG
10	2	R2,R5	3.9MΩ ±5%, SMD-1206	ERJ-8GEYJ395V	Panasonic - ECG
11	1	R3	3.6KΩ ±1%, SMD-0603	ERJ-3EKF3601V	Panasonic - ECG
12	1	R4	470KΩ ±5%, SMD-0805	ERJ-6GEYJ474V	Panasonic - ECG
13	1	R6	100Ω ±5%, SMD-0805	ERJ-6GEYJ101V	Panasonic - ECG
14	1	R7	16KΩ ±1%, SMD-0805	ERJ-6ENF1602V	Panasonic - ECG
15	1	R9	3.57Ω ±1%, SMD-0805	RC0805FR-073R57L	Yageo
16	1	R14	2.2KΩ ±5%, SMD-0805	ERJ-6GEYJ222V	Panasonic - ECG
17	1	D1	1A, 800V, rectifier bridge, ABS	ABS8	Taiwan Semiconductor
18	1	D2	1A, 1000V, fast recovery rectifier, 1206-S	SRGC10MH	ZOWIE
19	1	D6	1A, 200V, fast recovery rectifier, 1206-S	SRGC10DH	ZOWIE
20	1	D9	2A, 40V, schottky diode, DO-15	SR240	Won-Top Electronics
21	1	F1	10Ω, fusible resistor, 1W	FRM1WJT-52-10R	Yageo
22	1	L1	330μH, filter inductor, 0410	8230-80-RC	Bourns Inc.
23	1	FB1	10μH, chip inductor, SMD-0805	LQM21FN100M80L	Murata Electronics
24	1	T1	EE13, vertical(Renco Electronics, RLiw-1000)		

## 7.0 Transformer Drawing

### Schematic:

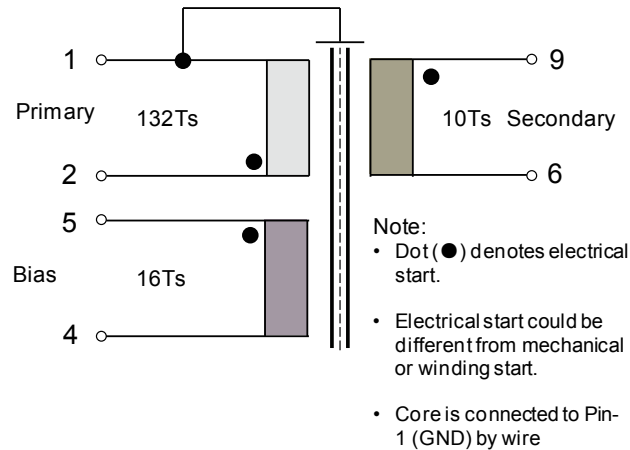

### Electrical Specifications:

1. Primary inductance ( $L_p$ ) = 2.4mH  $\pm$  (8%) @10KHz
2. Primary leakage inductance < 5% \*  $L_p$ , short pin7-pin10
3. Electrical strength = 3KV, 50/60Hz, 1min.

### Materials:

1. Core: EE13 (ferrite material TDK PC40 or equivalent)
2. Bobbin: EE13 vertical
3. Magnet wires (pri): type 2-UEW
4. Magnet wire (sec): triple insulated wires
5. Layer insulation tape: 3M1298 or equivalent

### Finished:

1. Varnish the complete assembly



## 8.0 Performance

### 8.1 Regulation, Ripple and Efficiency Measurement



\* Note: Output voltage is measured at end of PCB

$V_{IN}$ ( $V_{AC}$ )	$P_{IN}$ (W)	$V_{OUT}$ (V)	$I_{OUT}$ (mA)	$V_{RIPPLE}$ (mV <sub>P-P</sub> )	$P_{OUT}$ (W)	$\eta$ (%)	OCP (mA)	Average $\eta$ (%)
90	0.037	5.10	0	12			718	76.83
	1.008	5.11	150	28	0.77	76.04		
	1.969	5.12	300	36	1.54	78.01		
	2.982	5.12	450	40	2.30	77.26		
	4.049	5.13	600	52	3.08	76.02		
115	0.039	5.09	0	12			739	78.21
	1.006	5.11	150	28	0.77	76.19		
	1.952	5.12	300	40	1.54	78.69		
	2.920	5.13	450	36	2.31	79.06		
	3.908	5.14	600	40	3.08	78.92		
230	0.059	5.08	0	12			723	76.44
	1.059	5.14	150	28	0.77	72.80		
	2.014	5.12	300	44	1.54	76.27		
	2.968	5.13	450	36	2.31	77.78		
	3.908	5.14	600	40	3.08	78.92		
264	0.069	5.08	0	12			718	75.18
	1.091	5.14	150	28	0.77	70.67		
	2.042	5.12	300	40	1.54	75.22		
	3.008	5.13	450	60	2.31	76.75		
	3.949	5.14	600	40	3.08	78.10		

### 8.2 CV and CC Regulation

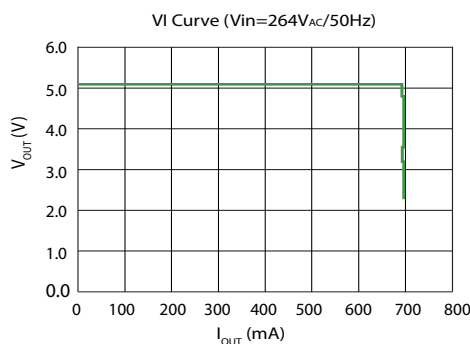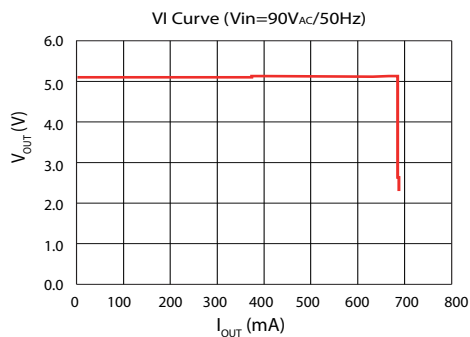

### 8.3 Conducted EMI

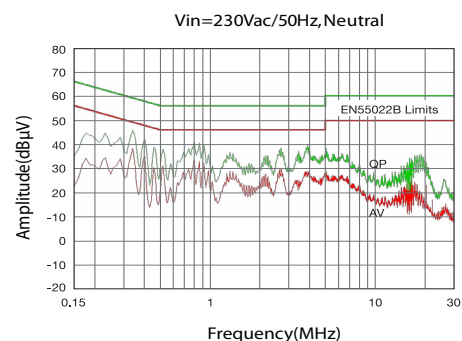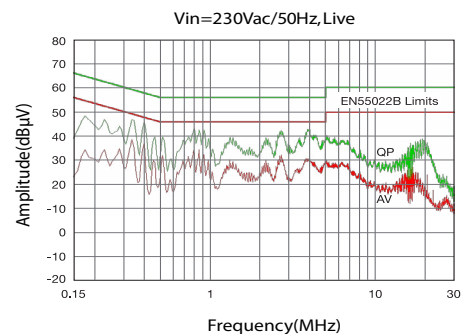

www.iwatt.com





## Trademark Information

© 2012 iWatt, Inc. All rights reserved. iWatt, BroadLED, **EZ-EMI**, Flickerless, Intelligent AC-DC and LED Power, and PrimAccurate are trademarks of iWatt, Inc. All other trademarks and registered trademarks are the property of their respective owners.

## Contact Information

**Web:** <http://www.iwatt.com>

**E-mail:** [info@iwatt.com](mailto:info@iwatt.com)

**Phone:** +1 (408) 374-4200

**Fax:** +1 (408) 341-0455

### iWatt Inc.

675 Campbell Technology Parkway, Suite 150  
Campbell, CA 95008

## Disclaimer

iWatt reserves the right to make changes to its products and to discontinue products without notice. The applications information, schematic diagrams, and other reference information included herein is provided as a design aid only and are therefore provided as-is. iWatt makes no warranties with respect to this information and disclaims any implied warranties of merchantability or non-infringement of third-party intellectual property rights.

iWatt cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in an iWatt product. No circuit patent licenses are implied.

Certain applications using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

IWATT SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR OTHER CRITICAL APPLICATIONS.

Inclusion of iWatt products in critical applications is understood to be fully at the risk of the customer. Questions concerning potential risk applications should be directed to iWatt, Inc.

iWatt semiconductors are typically used in power supplies in which high voltages are present during operation. High-voltage safety precautions should be observed in design and operation to minimize the chance of injury.

[www.iwatt.com](http://www.iwatt.com)